



电子科技大学
格拉斯哥学院
Glasgow College, UESTC

Score

Physical Experiment II

Prelab Report 15

Experiment Title: The Potentiometer

Student Number: 2017200602011

Chinese Name: 张立澄

Teaching Assistant: Hao Wen

Instructor: Jing Wu


Date: 2018.12.18

Score

Answers to Questions (20 points)

(1) We can't use the voltmeter to measure the emf of a cell. Because of the internal resistance of the battery, which means the measured terminal voltage is always lower than the EMF due to the current through the circuit and internal resistance of the battery. While the terminal voltage of a cell is the potential difference between its terminals.

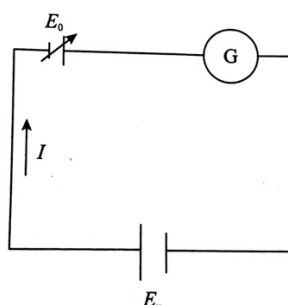(2) As shown in the figure below, the galvanometer G is a sensitive device capable of indicating the presence of very small current to indicate a condition of zero current accurately. When the deflection of the galvanometer is observed, adjust the emf of the standard cell until the galvanometer no longer deflects from zero, which means the galvanometer draws no current from the unknown source, and the magnitude of the unknown emf is equal to that of the standard cell.



(3) When the galvanometer reads zero, the current in the source circuit is equal to the current in the calibration circuit. Thus, we can obtain R by the Ohm's Law:

$$R = \frac{E_s}{I} = \frac{2.000V}{5.000mA} = 400\Omega$$

Since the resistor R_x doesn't draw any current in the measurement circuit. We can obtain the measured emf as following:

$$E_x = R_x I = 201.5\Omega \times 5.000mA = 1.0075V$$